



WEST BENGAL STATE UNIVERSITY
B.Sc. Honours 4th Semester Examination, 2023

PHSACOR10T-PHYSICS (CC10)

Time Allotted: 2 Hours

Full Marks: 40


*The figures in the margin indicate full marks.
Candidates should answer in their own words and adhere to the word limit as practicable.
All symbols are of usual significance.*

Question No. 1 is compulsory and answer any two from the rest


1. Answer any *ten* questions from the following:

2×10 = 20

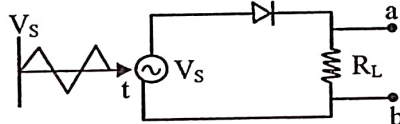- (a) For an unbiased p-n junction diode, sketch the variation of space charge, electric field and potential as a function of distance across the junction.
- (b) What is meant by diffusion capacitance of a p-n junction?
- (c) Can a voltmeter measure the built-in-barrier potential across the abrupt or step p-n junction?
- (d) What are the sources of instability of Q-point for CE amplifier?
- (e) Why do Si or Ge diodes not emit light but GaAs diodes do?
- (f) How can you use a bipolar junction transistor (BJT) as a switch?
- (g) Draw the waveform that will be shown in a CRO across a-b



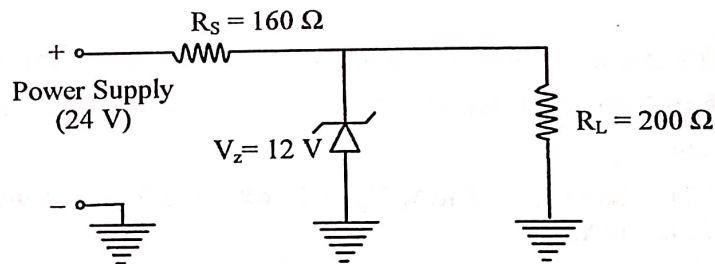- (h) In the Zener regulator circuit shown below, calculate current through the series resistance (R_S)



- (i) Why the noise behaviours of JFET is less than that of a BJT?
- (j) How is a power amplifier different from a voltage amplifier?
- (k) Explain the current-voltage characteristics of a solar cell.
- (l) A Zener diode with break-down voltage 6 V is connected in series with a 100Ω resistance and a load of $0.5k\Omega$ connected across the diode. The maximum allowable current through the Zener diode is 30 mA. Calculate the operating range of the input voltage.

- (m) If the input of an OPAMP integrator circuit is 1 volt then find and draw the nature of the output voltage. Assume $R = 1 \text{ M}\Omega$ and $C = 2 \mu\text{F}$.
- (n) An amplifier has a voltage gain of -100 and a feedback ratio of -0.04 . Find (i) the output voltage of the feedback amplifier for an input voltage of 60 mV and (ii) find the feedback voltage.
2. (a) A full wave rectifier is operated from 50 Hz supply with 60 V (r.m.s.). It is connected to a load drawing a current of magnitude 200 mA and using $100 \mu\text{F}$ filter capacitor. Calculate the d.c. output voltage and the r.m.s. value of ripple voltage. Also calculate the ripple factor. 1+2+2
- (b) Draw the circuit diagram of a logarithmic amplifier and a comparator using OPAMP and derive an expression for output voltage for the logarithmic amplifier. 1+2+2
3. (a) Draw a labeled circuit diagram of a two-stage R-C coupled amplifier. Find the mid-frequency gain of the amplifier with the help of an ac equivalent circuit. Explain why the gain of R-C coupled amplifiers falls at high frequencies. 2+3+2
- (b) A two-stage RC coupled amplifier uses transistors having h -parameters $h_{ie} = 1500 \Omega$ and $h_{fe} = 250$. If the load resistance is $10 \text{ k}\Omega$, find the value of the coupling capacitor for having a lower cut-off frequency of 10 Hz . 3
4. (a) Define "Slew rate". Find the input signal maximum frequency for a specified "Slew rate" of an OP-AMP. 1+2
- (b) Is an external input signal necessary for the output of an oscillator? If not, how are oscillations initiated? 2
- (c) Explain the working principle of Colpitts oscillator circuit using BJT. 5
5. (a) What are the fundamental differences between Class A and Class C amplifiers? 2
- (b) Negative feedback reduces the gain of an amplifier still this feedback is widely used, why? 2
- (c) What is JFET? An n -channel Si (having dielectric constant 12) JFET with a channel width of 0.06 cm is doped with a concentration $N_d = 10^{21} \text{ m}^{-3}$. Find the pinch off voltage. 1+3
- (d) An n channel FET has $I_{DSS} = 8 \text{ mA}$, $V_p = -4 \text{ volt}$. Find V_{GS} that will result in a drain current of 4.5 mA . 2

—x—